

---

Web Master Homepage

---

Hobby Electronics

---

Bristol Tri-Cities

---

AC Power Control with Arduino



## In Depth Look at AC Power Control with Arduino

by Lewis Loflin

- For related material see:
- [Hardware Interrupts Demo and Tutorial for ATMEGA168/Arduino](#)
- [Basic Triacs and SCRs](#)
- [Solid State AC Relays with Triacs](#)

In the above video and the code below we take an in depth look at the hardware for using Arduino interrupts to control AC power through a triac. Using a zero-crossing detector Arduino will detect the pulse then calculate a delay to control the power output to a load. The complete circuit schematic is [here](#).

For more on basic AC voltage see my video [Basic Electronic Power Supplies](#)


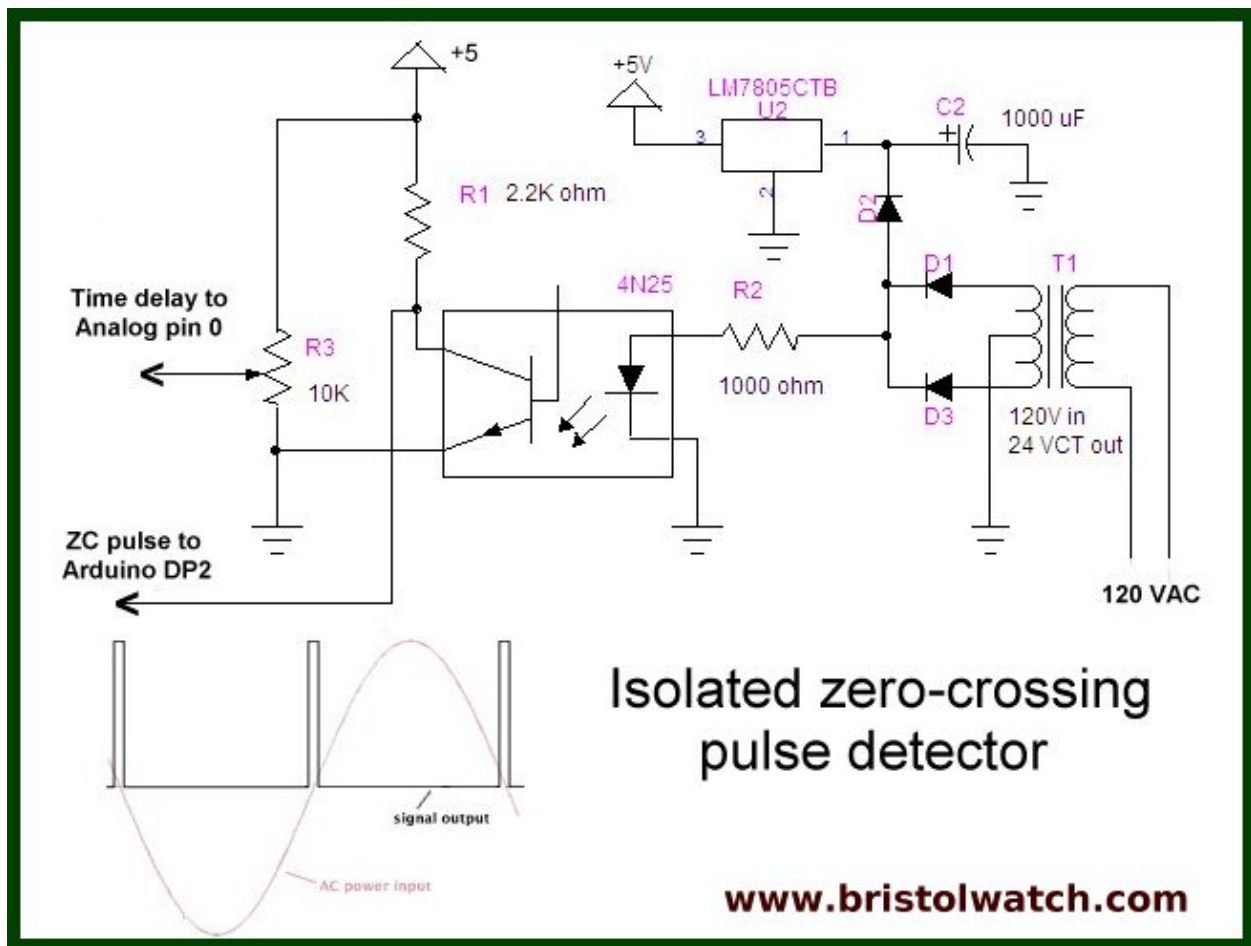



Fig. 1

Fig. 1 shows the 5-volt power supply for Arduino but includes blocking diode D2. On the cathode side we have filtered DC which is regulated to 5-volts through U2. On the Anode side we have unfiltered raw 120 Hz DC going to the LED in the 4N25 opto-coupler. The output from the photo-transistor collector goes to digital pin 2 of Arduino to interrupt 0. Potentiometer R3 goes analog pin 0 and is used to calculate the time delay for the triac firing pulses.

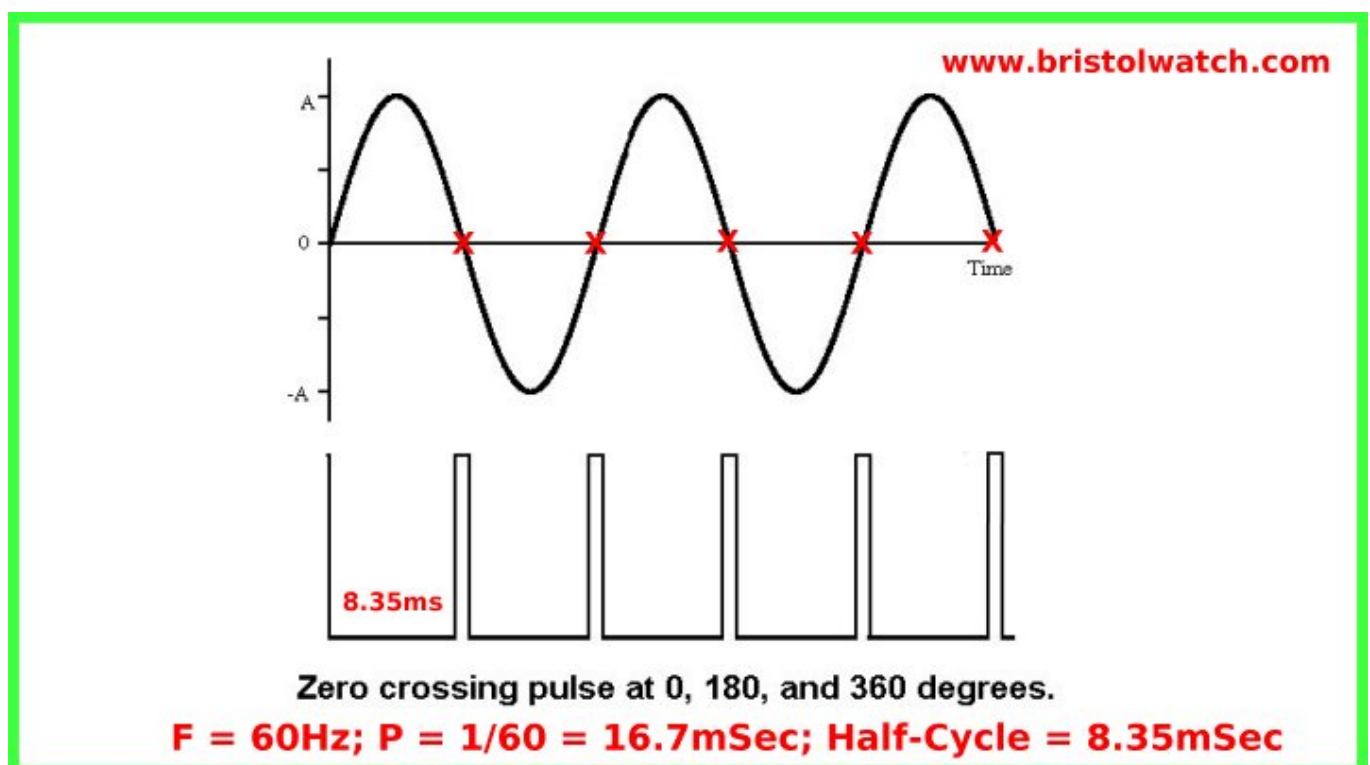

**Fig. 2**

Fig 2 shows the relationship of the zero-crossing pulse with the AC sine wave. By detecting the pulse and programming a delay one can control the power output level to a AC load.

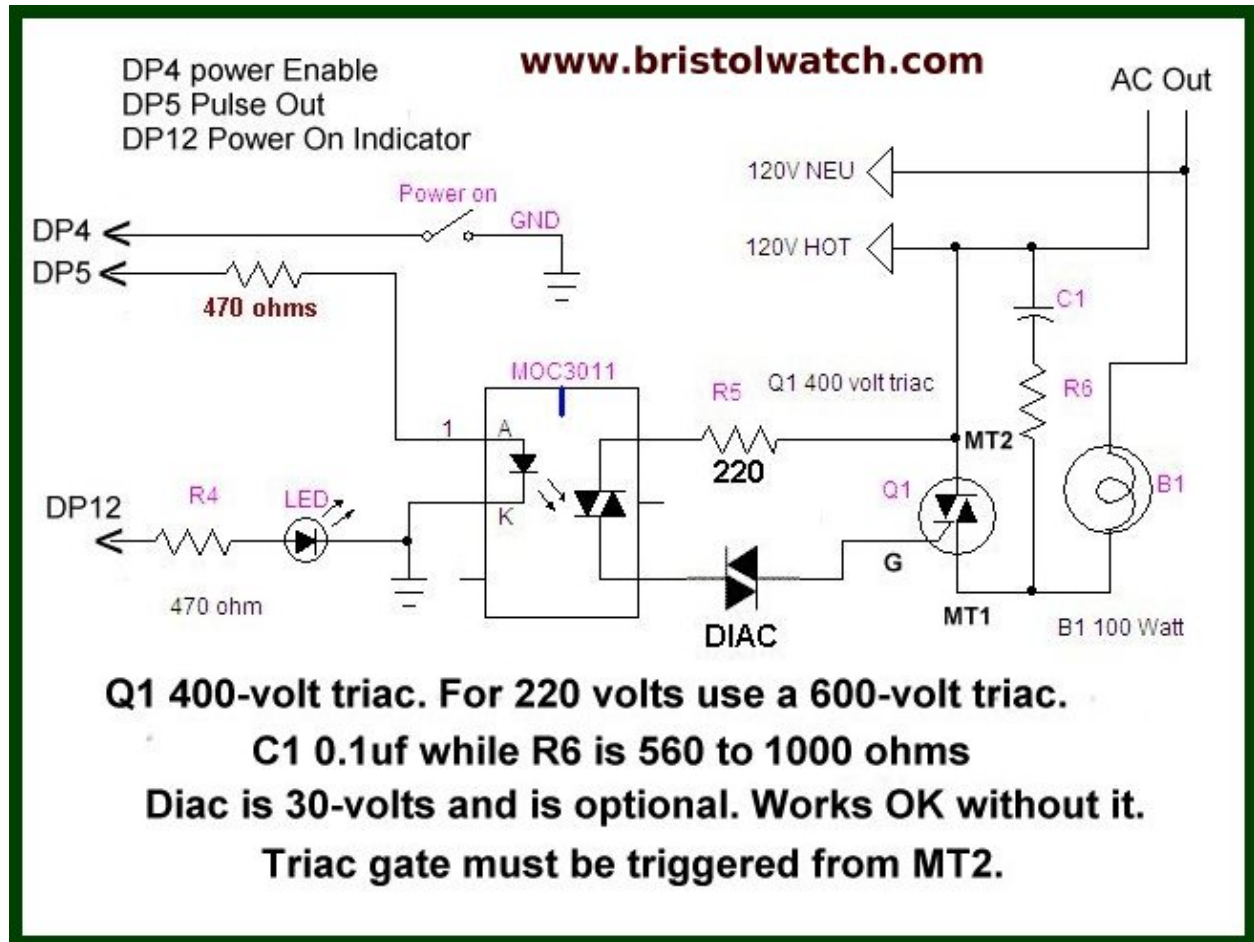

**Fig. 3**

Fig 3 shows the triac firing circuit. The MOC3011 opto-coupler uses a photo triac as opposed to a transistor. Pulses synchronized to the AC sinewave half-cycle are output from Arduino digital pin 5 to the LED in the MOC3011, which also serves to isolate the high voltage AC from the low-voltage components.

Pressing the power switch will enable trigger pulses to the MOC3011 while the LED on digital pin 12 is a power on indicator. C1 and R6 form a snubber circuit for inductive loads. Without a snubber switching noise from inductive loads will cause miss-firing of the triac.

# Machine Learning & MATLAB

Solve Common Technical Challenges. Download The Paper To Learn How. Go to [mathworks.com/Machine-Learning](https://mathworks.com/Machine-Learning)



/\*

**Purpose: to detect zero crossing pulse at INT0 digital pin 2, which after delay**

switches on a triac.

Power output to triac activated by external switch.

\*/

```
#define triacPulse 5
```

```
#define SW 4
```

```
#define aconLed 12
```

```
int val;
```

```
void setup() {
  pinMode(2, INPUT);
  digitalWrite(2, HIGH); // pull up
  pinMode(triacPulse, OUTPUT);
  pinMode(SW, INPUT);
  digitalWrite(SW, HIGH);
  pinMode(aconLed, OUTPUT);
  digitalWrite(aconLed, LOW);
}
```

```
void loop() {
  // check for SW closed
  if (!digitalRead(SW)) {
    // enable power
    attachInterrupt(0, acon, FALLING);
    // HV indicator on
    digitalWrite(aconLed, HIGH);
  } // end if
  else if (digitalRead(SW)) {
    detachInterrupt(0); // disable power
    // HV indicator off
    digitalWrite(aconLed, LOW);
  } // else
} // end loop
```

```
// begin AC interrupt routine
```

```
// delay() will not work!
```

```
void acon()
```

```
{
  delayMicroseconds((analogRead(0) * 6) + 1000); // read AD1
  digitalWrite(triacPulse, HIGH);
  delayMicroseconds(200);
  // delay 200 uSec on output pulse to turn on triac
  digitalWrite(triacPulse, LOW);
}
```

- [Hardware Interrupts Tutorial for Arduino](#)
- [Basic Triacs and SCRs](#)
- [Solid State AC Relays with Triacs](#)
- [Light Activated Silicon Controlled Rectifier \(LASCR\)](#)
- [Arduino AC Power Control Using Interrupts](#)
- [In Depth Look at AC Power Control with Arduino](#)
- [Testing the Keyes IR Sensor Module with Arduino](#)
- [How to Connect Easy Driver Micro-Stepper Controller to Arduino](#)

- [Connect Arduino to LCD Display with 74164 Shift Register](#)
- [Arduino with LCD Display and DS18B20 Temperature Sensor](#)
- Below has differing code from the above. Works the same.
- [Arduino with LCD Display and DHT11 Temperature-Humidity Sensor](#)
- [In Depth Look at AC Power Control with Arduino](#)
- Four part series:
- [Experimenting with the PCA9555 32-Bit GPIO Expander with Arduino](#)
- [PCA9555 32-Bit GPIO Expander with Arduino and a 4X4 Keypad](#)
- [PCA9555 32-Bit GPIO Expander with Arduino Using Interrupts](#)
- [PCA9555 32-Bit GPIO Expander with Arduino and LCD Display](#)
- [YouTube Video Interfacing PCA9555 to Arduino](#)

## Stepper Motors

- [Considerations for Using Stepper Motors](#)
- [How to Connect Easy Driver Micro-Stepper Controller to Arduino](#)
- [Using a Unipolar Stepper Motor with a Arduino](#)
- [Using the MC3479 Stepper Motor Controller with Arduino](#)
- [Connecting the Arduino to a L298N H-Bridge](#)
- [L298N Motor Controller Theory and Projects](#)
- [Arduino stepper motor control](#) YouTube
- Quick navigation main page:
- [Arduino Microcontroller Projects](#)
- [General Electronics Learning and Projects](#)
- [Raspberry Pi and Linux](#)
- [Connecting a PC Printer Port to Electronics with Python](#)
- [Microchip PIC 18F2550](#)
- [PICAXE Microcontroller](#)
- [Gen. Electronics](#)
- [My YouTube Channel](#)
- [Raspberry Pi & Linux](#)
- [Arduino Projects](#)
- [PIC18F2550 in C++](#)
- [PIC16F628A in Assembly](#)
- [PICAXE Projects](#)
- [Web Master](#)
- [Bristol VA/TN](#)
- [E-Mail](#)
- [Environmentalism](#)
- [US Constitution](#)
- [Religious Themes 1](#)
- [Religious Themes 2](#)

[website hits counter](#)

389736

